# **CAPACITORS**

#### Introduction to Capacitors

The capacitor is a widely used electrical component:

- Storing energy eg in power supplies and camera flash circuit
- Timing for example with a 555 timer IC controlling the charging and discharging;
- Smoothing eg in a power supply;
- Coupling eg between stages of an audio system and a loudspeaker;
- Filtering eg in the tone control of an audio system;
- Tuning eg in a radio system;
- Decoupling in logic circuits for prevent spikes and ripple on the supply lines

#### Capacitors

- A capacitor is a device that has the ability to store a quantity of static electricity.
- In its simplest form a capacitor consists of two plates which are separated by an insulating material known as a **dielectric**.
- The charge Q stored in a capacitor is given by:

$$Q = I \times t$$
 coulombs

 where I is the current in amperes and t the time in seconds.





#### Capacitance

- It is the property of a capacitor to store an electric charge when its plates are at different potentials.
- The unit of capacitance is termed the farad (F) which may be defined as the capacitance of a capacitor between the plates of which there appears a potential difference of 1 volt when it is charged by 1 coulomb of electricity.
- Hence:

$$C = \frac{Q}{V}$$

A direct current of 4 A flows into a previously uncharged 20  $\mu$ F capacitor for 3 ms. Determine the p.d. between the plates.

$$I = 4 \text{ A}$$
;  $C = 20 \text{ } \mu\text{F} = 20 \times 10^{-6} \text{ F}$ ;  $t = 3 \text{ ms} = 3 \times 10^{-3} \text{ s}$   
 $Q = It = 4 \times 3 \times 10^{-3} \text{ C}$   
 $V = \frac{Q}{C} = \frac{4 \times 3 \times 10^{-3}}{20 \times 10^{-6}} = \frac{12 \times 10^{6}}{20 \times 10^{3}} = 0.6 \times 10^{3} = 600 \text{ V}$ 

A 5  $\mu$ F capacitor is charged so that the p.d. between its plates is 800 V. Calculate how long the capacitor can provide an average discharge current of 2 mA.

$$C = 5 \text{ } \mu\text{F} = 5 \times 10^{-6} \text{ F}; V = 800 \text{ V}; I = 2 \text{ mA} = 2 \times 10^{-3} \text{ A}$$


$$Q = CV = 5 \times 10^{-6} \times 800 = 4 \times 10^{-3} \text{ C}$$
Also,  $Q = It$ . Thus,  $t = \frac{Q}{I} = \frac{4 \times 10^{-3}}{2 \times 10^{-3}} = 2 \text{ s}$ 

# Parallel plate capacitor

 For a parallel plate capacitor, capacitance C is proportional to the area A of a plate, inversely proportional to the plate spacing d (i.e. the dielectric thickness) and depends on the nature of the dielectric:

Capacitance 
$$C = \frac{\varepsilon_0 \varepsilon_r A}{d}$$
 farads

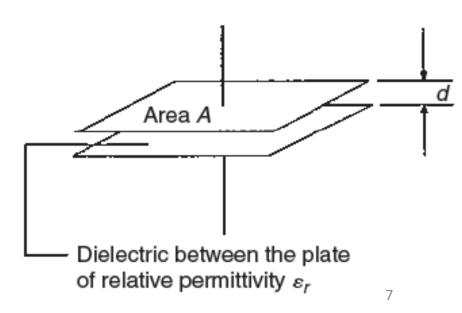
- where  $\varepsilon_0 = 8.85 \times 10 12$  F/m (constant)
- $\varepsilon_r$  = relative permittivity
- A = area of one of the plates in m2 and
- d = thickness of dielectric in m.


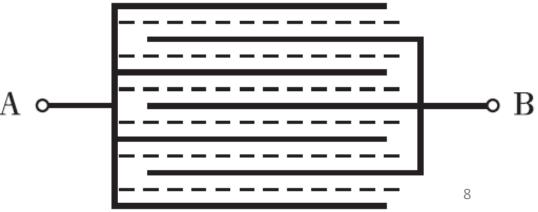
# Capacitance of a multi-plate capacitor

- The capacitance can be increased by interleaving several plates.
- In the figure, 7 plates are shown, forming 6 capacitors with a capacitance 6 times that of one pair of plates.
- If such an arrangement has n plates then capacitance  $C \propto (n-1)$ .

Capacitance = 
$$\frac{\epsilon_0 \epsilon_r (n-1)A}{d}$$
 farads



(a) A ceramic capacitor has an effective plate area of 4cm<sup>2</sup> separated by 0.1mm of ceramic of relative permittivity 100. Calculate the capacitance of the capacitor in picofarads.

Capacitance 
$$C = \frac{\varepsilon_0 \varepsilon_r A}{d}$$
 farads  

$$= \frac{8.85 \times 10^{-12} \times 100 \times 4 \times 10^{-4}}{0.1 \times 10^{-3}} F$$

$$= \frac{8.85 \times 4}{10^{10}} F = \frac{8.85 \times 4 \times 10^{12}}{10^{10}} pF$$

$$= 3540 pF$$

# Example

(b) If the capacitor in part (a) is given a charge of  $1.2\mu\text{C}$ , what will be the p.d. between the plates?

$$Q = CV$$
 thus  $V = \frac{Q}{C} = \frac{1.2 \times 10^{-6}}{3540 \times 10^{-12}}$ 

$$V = 339 \text{ V}$$

A capacitor is made with 7 metal plates and separated by sheets of mica having a thickness of 0.3 mm and a relative permittivity of 6. The area of one side of each plate is 500 cm2. Calculate the capacitance in microfarads.

$$\therefore \quad \text{Capacitance} = \frac{\epsilon_0 \epsilon_r (n-1) A}{d} \quad \text{farads}$$

$$C = \frac{8.85 \times 10^{-12} \times 6 \times 6 \times 0.05}{0.0003} = 0.0531 \times 10^{-6} \text{ F}$$
$$= 0.053 \ \mu\text{F}$$

# Capacitors connected in parallel


• Since the current divides, the total charge ( $Q_T = I \times t$ ) is also divided between the three capacitors.  $Q_T = Q_1 + Q_2 + Q_3$ 

• But 
$$Q_T = CV$$
,  $Q_1 = C_1V$ ,  $Q_2 = C_2V$  and  $Q_3 = C_3V$ 

where C is the total equivalent circuit Capacitance:

$$CV = C_1V + C_2V + C_3V$$
$$C = C_1 + C_2 + C_3$$

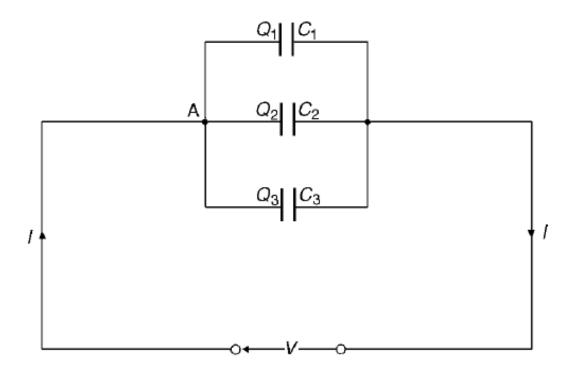• Note that this remarks similar to that used for **resistors** connected in **series** 




# Capacitors connected in series

- Let the p.d. across the individual capacitors be  $V_1$ ,  $V_2$  and  $V_3$  and the charge on each capacitor is found to be the same, Q coulombs.
- In a series circuit:  $V = V_1 + V_2 + V_3$  Since  $V = \frac{Q}{C}$  then  $\frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$
- where C is the total equivalent circuit capacitance, thus  $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$
- Note that this formula is similar to that used for resistors connected in parallel
- For the special case of two capacitors

in series: 
$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{C_2 + C_1}{C_1 C_2}$$

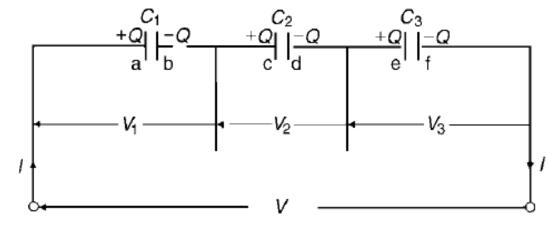Hence 
$$C = \frac{C_1 C_2}{C_1 + C_2}$$
 (i.e.  $\frac{\text{product}}{\text{sum}}$ )



- Calculate the equivalent capacitance of two capacitors of 6  $\mu F$  and 4  $\mu F$  connected (a) in parallel and (b) in series
- (a) In parallel, equivalent capacitance  $C = C1 + C2 = 6 \mu F + 4 \mu F = 10 \mu F$
- (b) In series, equivalent capacitance C is given by:

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

$$C = \frac{6 \times 4}{6 + 4} = \frac{24}{10} = 2.4 \ \mu F$$

Capacitances of 1  $\mu$ F, 3  $\mu$ F, 5  $\mu$ F and 6  $\mu$ F are connected in parallel to a direct voltage supply of 100 V. Determine

(a) the equivalent circuit capacitance,

$$C = C_1 + C_2 + C_3 + C_4$$
  
 $C = 1 + 3 + 5 + 6 = 15 \mu F$ 

(b) the total charge

Total charge  $Q_T = CV$ 

$$Q_T = 15 \times 10^{-6} \times 100 = 1.5 \times 10^{-3} C = 1.5 \text{ mC}$$

(c) the charge on each capacitor

$$Q_{1} = C_{1}V = 1 \times 10^{-6} \times 100$$

$$= 0.1 \text{ mC}$$

$$Q_{2} = C_{2}V = 3 \times 10^{-6} \times 100$$

$$= 0.3 \text{ mC}$$

$$Q_{3} = C_{3}V = 5 \times 10^{-6} \times 100$$

$$= 0.5 \text{ mC}$$

$$Q_{4} = C_{4}V = 6 \times 10^{-6} \times 100$$

$$= 0.6 \text{ mC}$$

$$Q_T = Q_1 + Q_2 + Q_3 + Q_4$$
  
= 1.5 mC

Capacitances of 3 µF, 6 µF and 12 µF are connected in series across a 350 V supply. Calculate (a) the equivalent circuit capacitance,

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$
i.e. 
$$\frac{1}{C} = \frac{1}{3} + \frac{1}{6} + \frac{1}{12} = \frac{4+2+1}{12} = \frac{7}{12}$$

$$C = \frac{12}{7} = 1\frac{5}{7} \mu F$$

(b) the charge on each capacitor:

$$Q_T = CV$$
,  
 $Q_T = \frac{12}{7} \times 10^{-6} \times 350 = 600 \ \mu\text{C} \text{ or } 0.6 \ \text{mC}$ 

Since the capacitors are in series 0.6 mC is the charge on each.

(c) the pd across each capacitor.

$$V_{1} = \frac{Q}{C_{1}} = \frac{0.6 \times 10^{-3}}{3 \times 10^{-6}}$$

$$= 200 \text{ V}$$

$$V_{2} = \frac{Q}{C_{2}} = \frac{0.6 \times 10^{-3}}{6 \times 10^{-6}}$$

$$= 100 \text{ V}$$

$$V_3 = \frac{Q}{C_3} = \frac{0.6 \times 10^{-3}}{12 \times 10^{-6}}$$
$$= 50 \text{ V} \text{ 15}$$

# Dielectric strength

The maximum amount of field strength that a dielectric can withstand is called the dielectric strength of the material.

$$E_m = \frac{V_m}{d}$$

#### **Energy stored**

• The energy, W, stored by a capacitor is given by

$$W = \frac{1}{2} CV^2$$
 joules

# **Energy stored**

**Example:** Determine the energy stored in a  $3\mu F$  capacitor when charged to 400V. (b) Find also the average power developed if this energy is dissipated in a time of 10  $\mu s$ .

(a) Energy stored 
$$W = \frac{1}{2}CV^2$$
 joules  

$$= \frac{1}{2} \times 3 \times 10^{-6} \times 400^2$$

$$= \frac{3}{2} \times 16 \times 10^{-2}$$

$$= 0.24 \text{ J}$$
(b) Power =  $\frac{\text{Energy}}{\text{time}} = \frac{0.24}{10 \times 10^{-6}} \text{ W} = 24 \text{ kW}$ 

# Discharging a Capacitor

- When a capacitor has been disconnected from the supply it may still be charged and it may retain this charge for some considerable time.
- Thus precautions must be taken to ensure that the capacitor is automatically discharged after the supply is switched off.
- This is done by connecting a high-value resistor across the capacitor terminals.