

# Simple DC circuits

# Main effects of electric current

There are three main effects of an electric current:


1. **Magnetic effect:** bells, relays, motors, generators, transformers, telephones, car-ignition and lifting magnets
2. **Chemical effect** :primary and secondary cells and electroplating
3. **Heating effect:** cookers, water heaters, electric fires, irons, furnaces

# **Simple DC circuits**

1. Series circuit
2. Parallel circuit


# Series circuits

- Series circuits diagram

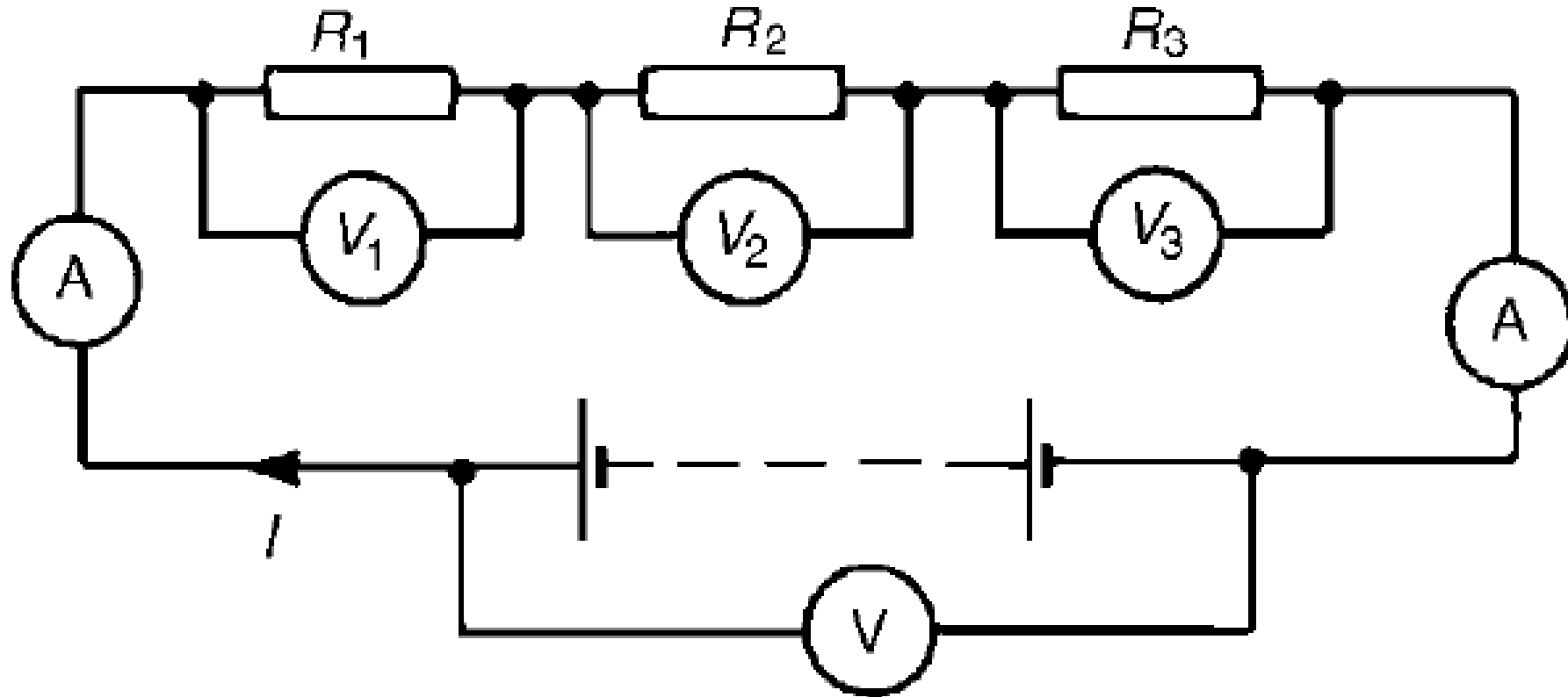
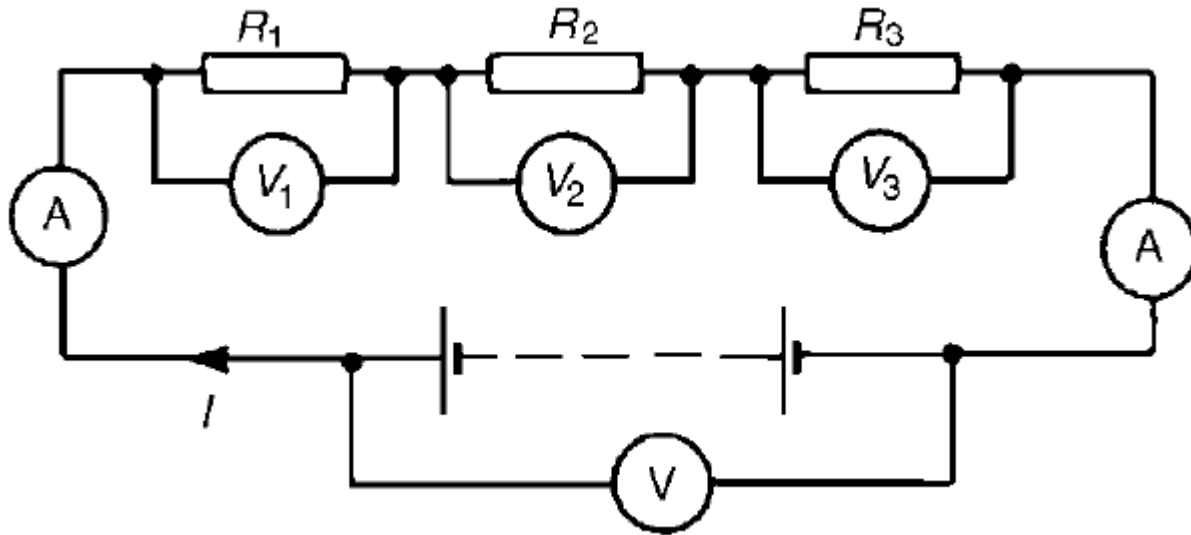
# Series circuits

- Resistors  $R_1$ ,  $R_2$  and  $R_3$  connected end to end.
- The current  $I$  is the same in all parts of the circuit
- the sum of the voltages  $V_1$ ,  $V_2$  and  $V_3$  is equal to the total applied voltage,  $V$ , i.e.  $V = V_1 + V_2 + V_3$




# Series circuits

From Ohm's law:

- $V_1 = IR_1$ ,  $V_2 = IR_2$ ,  $V_3 = IR_3$  and  $V = IR$   
where  $R$  is the total circuit resistance.
- Since  $V = V_1 + V_2 + V_3$
- then  $IR = IR_1 + IR_2 + IR_3$
- Dividing throughout by  $I$  gives:


$$R = R_1 + R_2 + R_3$$

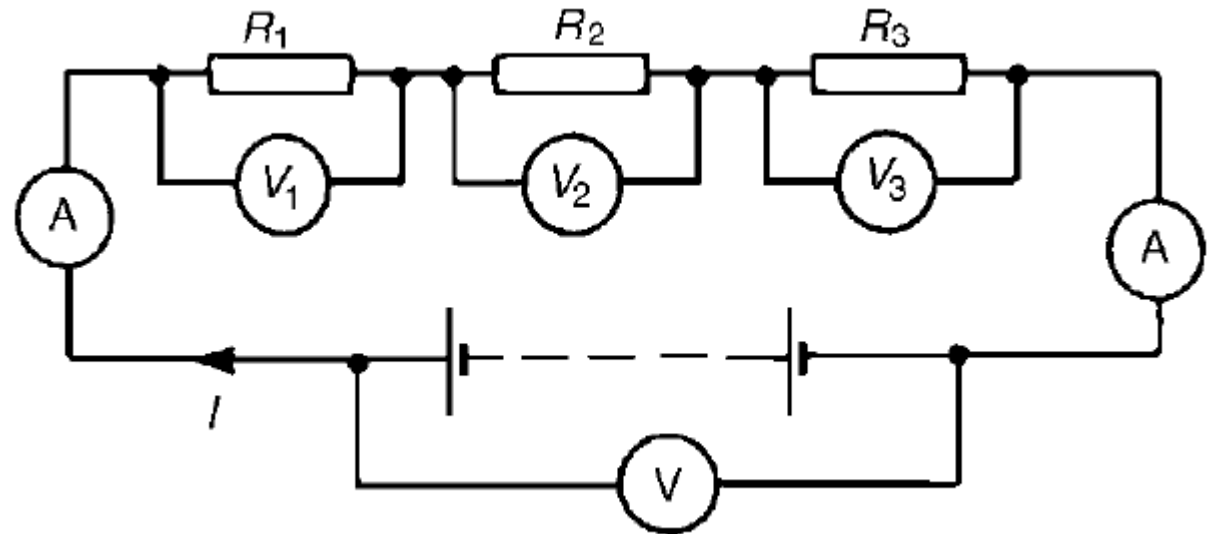

# Series circuits

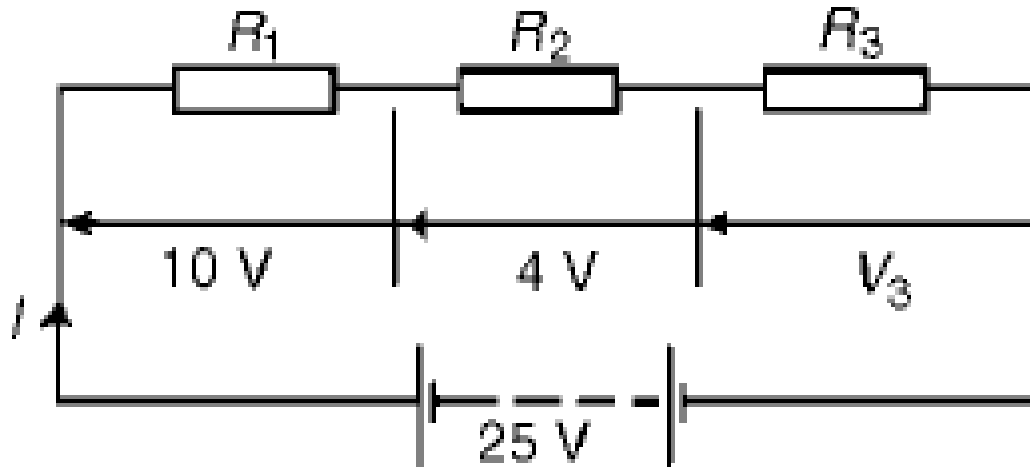Example:

For the circuit shown in Figure below, determine the p.d. across resistor  $R_3$ . If the total resistance of the circuit is 100, determine the current flowing through resistor  $R_1$ . Find also the value of resistor  $R_2$ .



# Series circuits

Example:

$$\text{P.d. across } R_3, V_3 = 25 - 10 - 4 = 11 \text{ V}$$

$$\text{Current } I = \frac{V}{R} = \frac{25}{100} = 0.25 \text{ A, which is the current flowing in each resistor}$$

$$\text{Resistance } R_2 = \frac{V_2}{I} = \frac{4}{0.25} = 16 \Omega$$




# Series circuits

Four resistors are connected in series with  $R_1=82\Omega$ ,  $R_2=45\Omega$ ,  $R_3=23\Omega$  and  $R_4=50\Omega$ . The supply voltage is 50 volts. (i) draw a well labelled circuit diagram (ii) determine

- (a) The total circuit resistance
- (b) The supply current
- (c) Voltage across each resistor
- (d) The power dissipated in  $R_2$
- (e) Energy consumed by the circuit
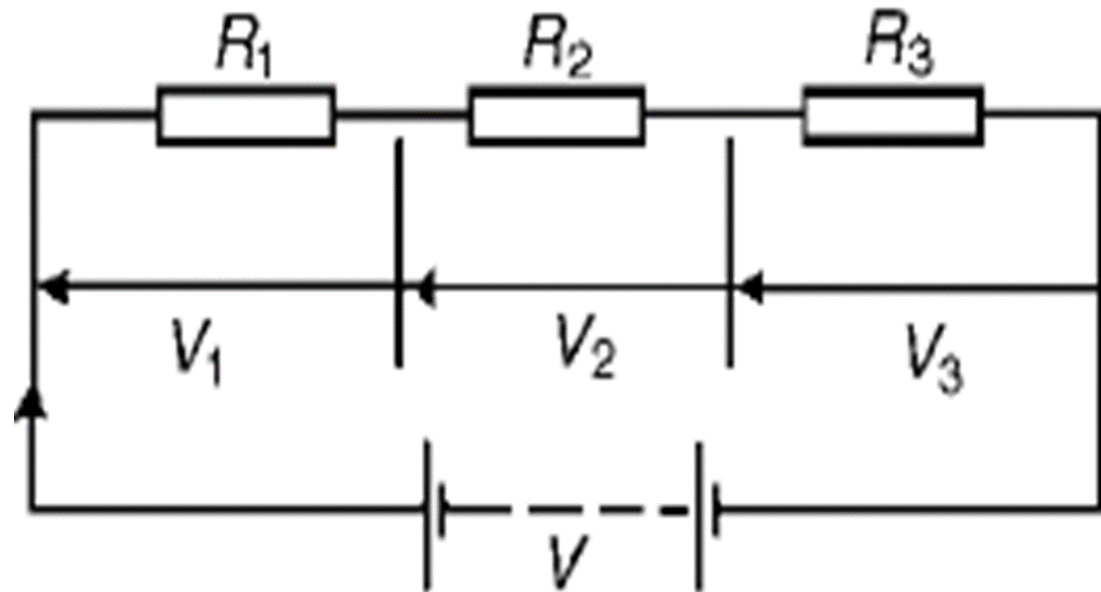
# Series circuits


- For the circuits shown in the figure, given that  $V_1=5$  Volts ,  $V_2=2$  Volts and  $V_3=6$  Volts and supply current =4 amps. Determine (a) Battery voltage (b) Total circuit resistance (c) Values of resistance of resistors  $R_1$ ,  $R_2$  and  $R_3$ .



# Series circuits
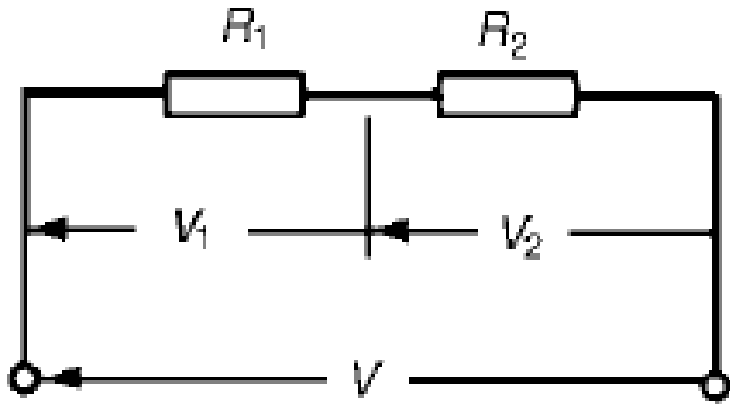
## Potential divider

- The ratio of the voltages depends on the ratio of the resistances.
- Potential (voltage) divider.



$$V_1 = \left( \frac{R_1}{R_1 + R_2} \right) V$$


$$V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V$$

# Series circuits

## Potential divider

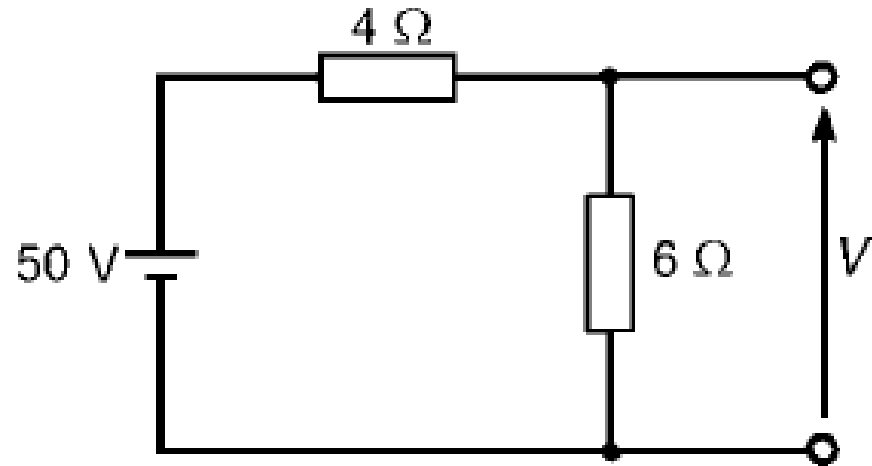Example:

Determine the value of voltage  $V$  shown in Figure below




# Series circuits

## Potential divider

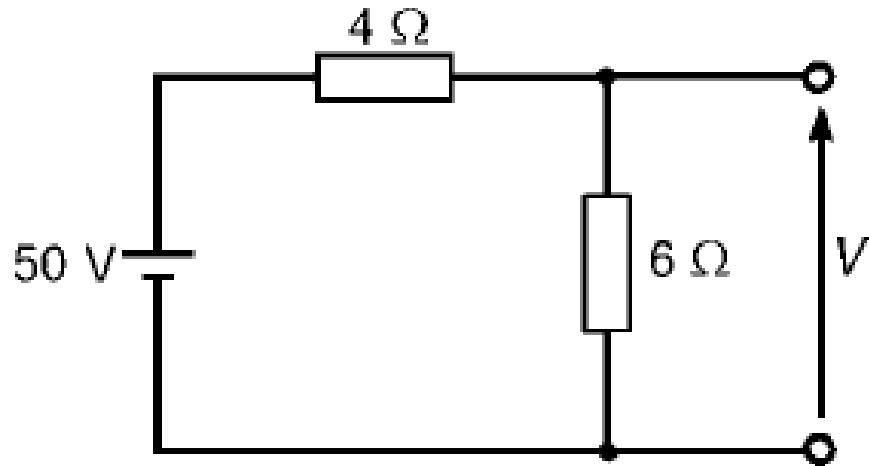Example:

Determine the value of voltage  $V$  shown in Figure below



$$V = \left( \frac{6}{6 + 4} \right) (50) = 30 \text{ V}$$

# Parallel circuits

- the sum of the currents  $I_1$ ,  $I_2$  and  $I_3$  is equal to the total circuit current,  $I$ , i.e.  $I = I_1 + I_2 + I_3$ , and the source p.d.,  $V$  volts, is the same across each of the resistors.
- From Ohm's law:

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3} \text{ and } I = \frac{V}{R}$$


where  $R$  is the total circuit resistance.

- Since  $I = I_1 + I_2 + I_3$

$$\text{then, } \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

- Dividing throughout by  $V$  gives:
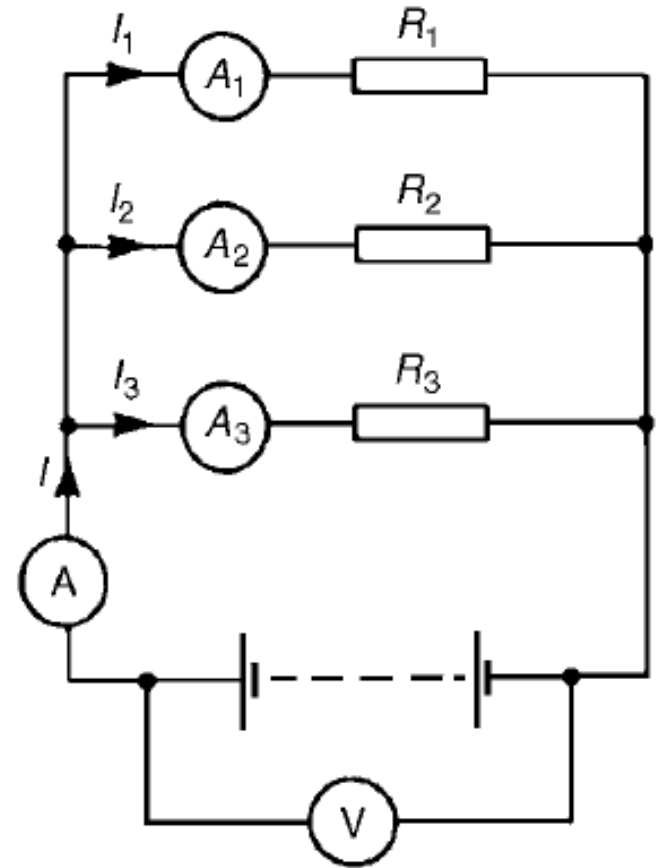
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$




# Two Resistors in parallel

For only two resistors in parallel:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$

Hence  $\boxed{R = \frac{R_1 R_2}{R_1 + R_2}}$  (i.e.  $\frac{\text{product}}{\text{sum}}$ )

# Current division

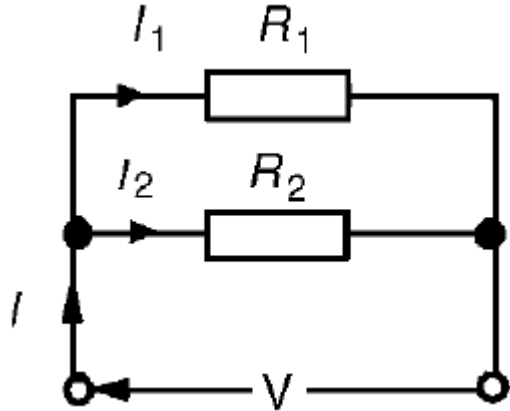

- For the circuit the total circuit resistance,  $R_T$  is given by:

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{and } V = IR_T = I \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\text{Current } I_1 = \frac{V}{R_1} = \frac{I}{R_1} \left( \frac{R_1 R_2}{R_1 + R_2} \right) = \left( \frac{R_2}{R_1 + R_2} \right) (I)$$

$$\text{current } I_2 = \frac{V}{R_2} = \frac{I}{R_2} \left( \frac{R_1 R_2}{R_1 + R_2} \right) = \left( \frac{R_1}{R_1 + R_2} \right) (I)$$

$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) (I)$$


$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) (I)$$



# Parallel circuit

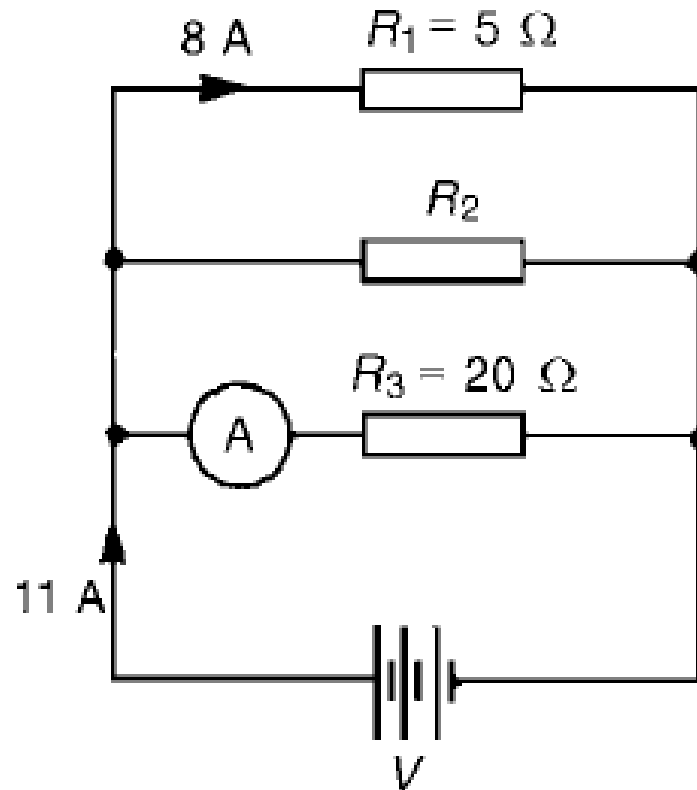Example:


For the circuit shown in Figure below determine (a) the reading on the ammeter, and (b) the value of resistor  $R_2$ .



# Parallel circuit

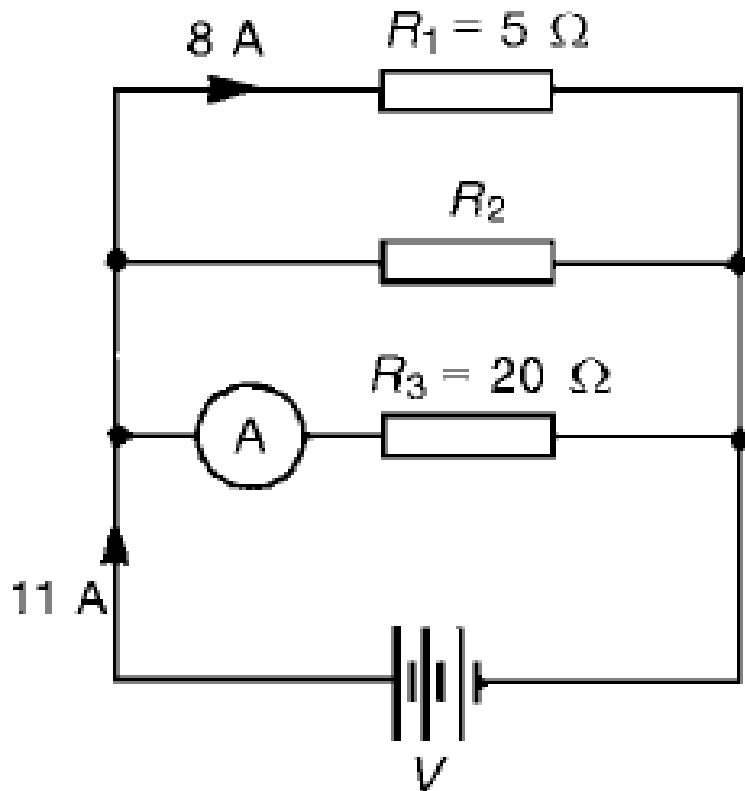Example:

For the circuit shown in Figure below determine (a) the reading on the ammeter, and (b) the value of resistor  $R_2$ .



P.d. across  $R_1$  is the same as the supply voltage  $V$ .

Hence supply voltage,  $V = 8 \times 5 = 40 \text{ V}$


(a) Reading on ammeter,  $I = \frac{V}{R_3} = \frac{40}{20} = 2 \text{ A}$

(b) Current flowing through  $R_2 = 11 - 8 - 2 = 1 \text{ A}$

Hence,  $R_2 = \frac{V}{I_2} = \frac{40}{1} = 40 \Omega$

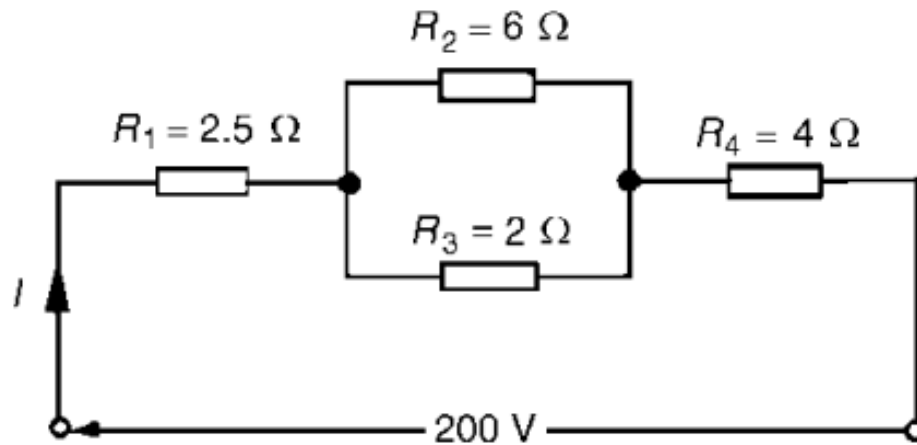
# Example

For the series-parallel arrangement shown in Figure , find (a) the supply current, (b) the current flowing through each resistor and (c) the p.d. across each resistor.



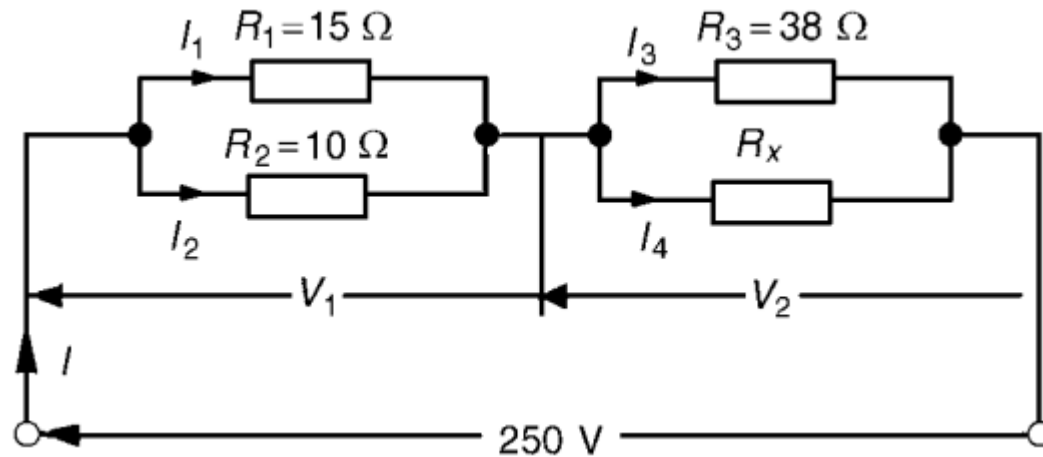
# Example

For the circuit shown in Figure calculate (a) the value of resistor  $R_x$  such that the total power dissipated in the circuit is 2.5 kW, and (b) the current flowing in each of the four resistors.



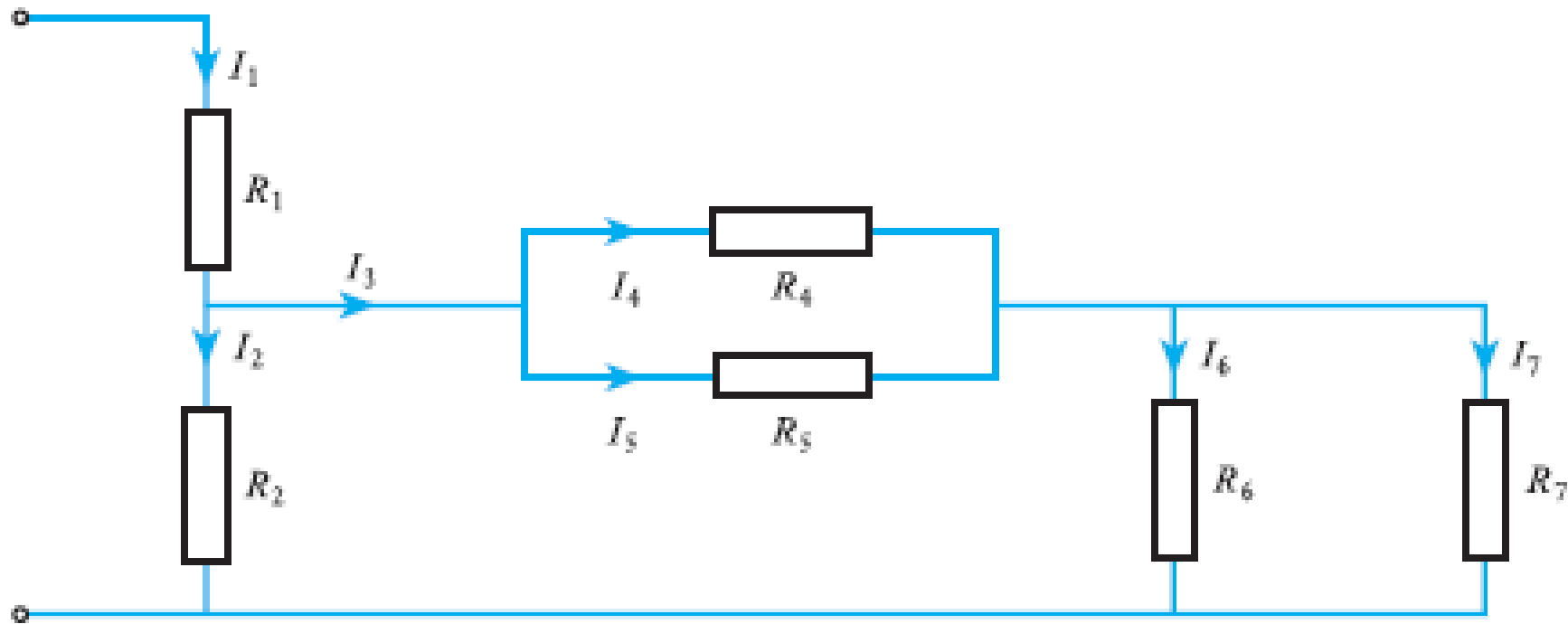
# Series-parallel networks

- $R_4$  is in parallel with  $R_5$  and  $R_6$  is in parallel with  $R_7$ .
- The network comprising  $R_4$  and  $R_5$  is in series with the network comprising  $R_6$  and  $R_7$ .
- $R_2$  is in parallel with the network comprising  $R_4$ ,  $R_5$ ,  $R_6$  and  $R_7$  and  $R_1$  in series with that combination


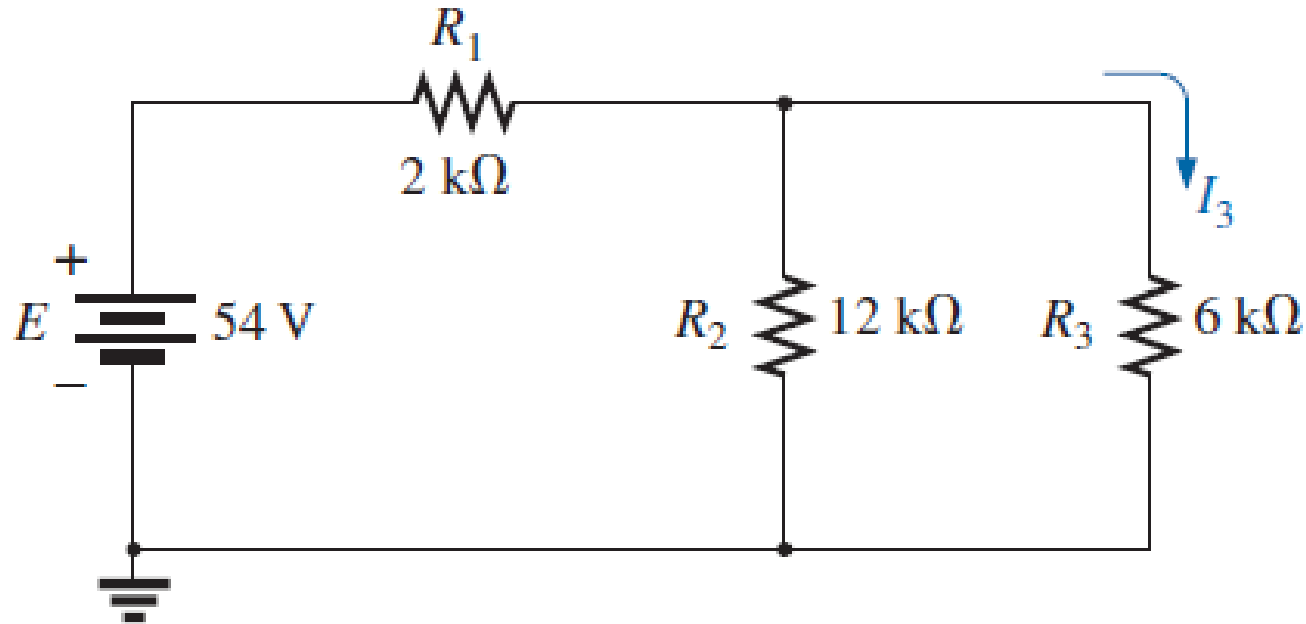
# Example of series-parallel

- Find current  $I_3$  for the series-parallel network



# Example of series-parallel

- $R_2$  and  $R_3$  are in parallel, their total resistance is

$$R' = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{(12 \text{ k}\Omega)(6 \text{ k}\Omega)}{12 \text{ k}\Omega + 6 \text{ k}\Omega} = 4 \text{ k}\Omega$$

Resistors  $R_1$  and  $R'$  are then in series, resulting in a total resistance of:


$$R_T = R_1 + R' = 2 \text{ k}\Omega + 4 \text{ k}\Omega = 6 \text{ k}\Omega$$

- The source current is then determined using Ohm's law:  $I_s = \frac{E}{R_T} = \frac{54 \text{ V}}{6 \text{ k}\Omega} = 9 \text{ mA}$
- since  $R_1$  and  $R'$  are in series, they have the same current  $I_s$ :  $I_1 = I_s = 9 \text{ mA}$
- $I_1$  is the total current entering the parallel combination of  $R_2$  and  $R_3$ . Applying the current divider rule :

$$I_3 = \left( \frac{R_2}{R_2 + R_3} \right) I_1 = \left( \frac{12 \text{ k}\Omega}{12 \text{ k}\Omega + 6 \text{ k}\Omega} \right) 9 \text{ mA} = 6 \text{ mA}$$
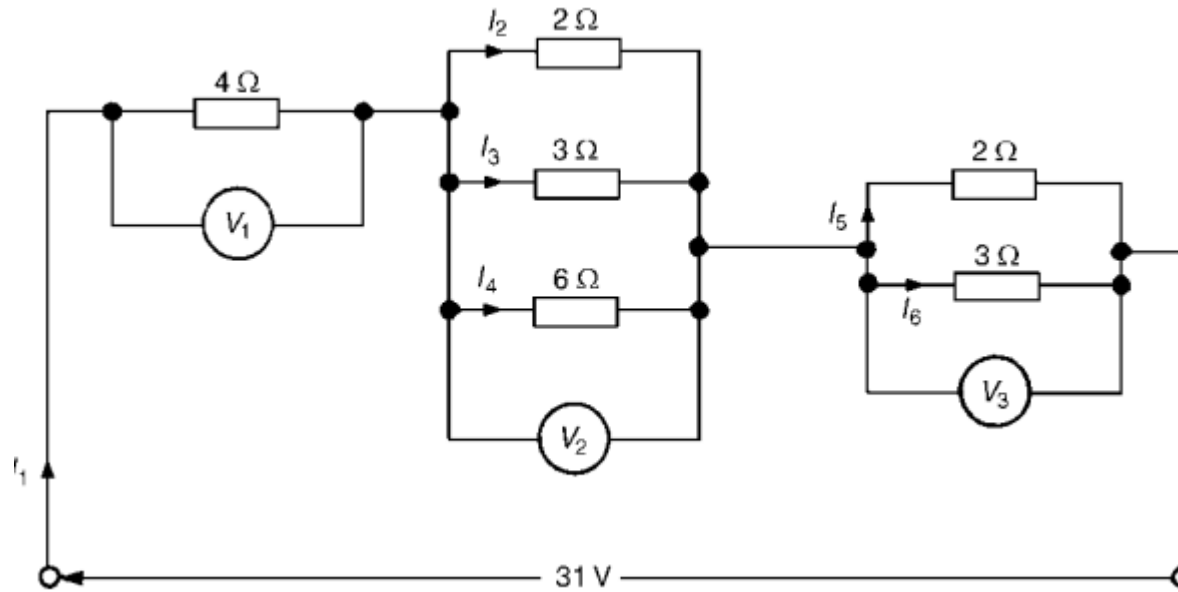
# EXAMPLE


- Determine the currents and voltages indicated in the circuit shown in Figure






# EXAMPLE

•

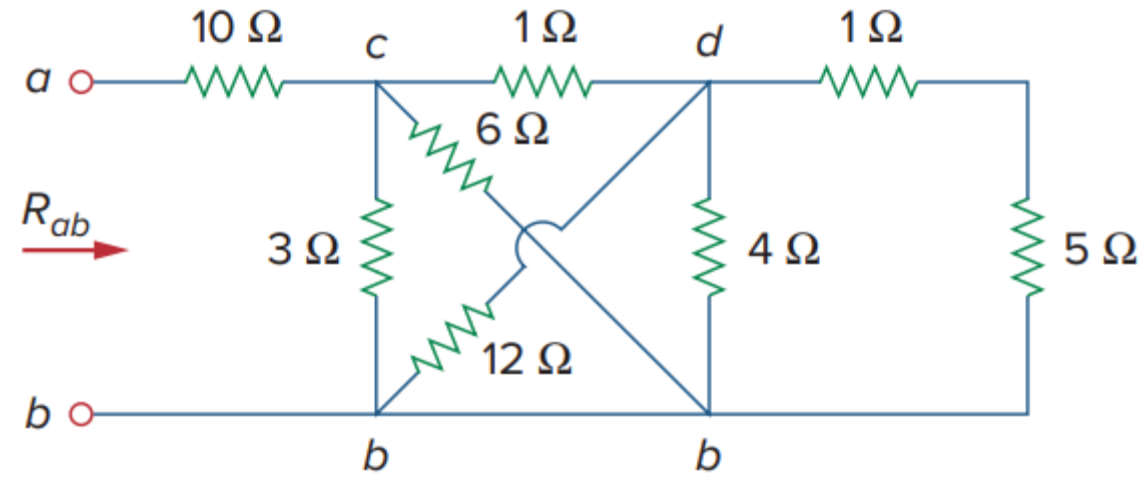


# EXAMPLE

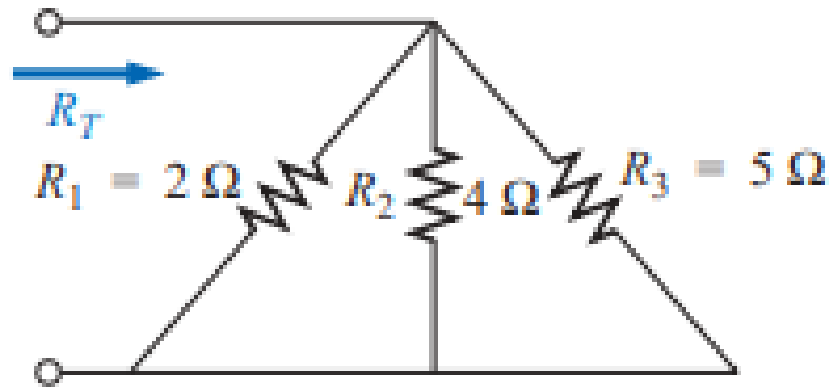

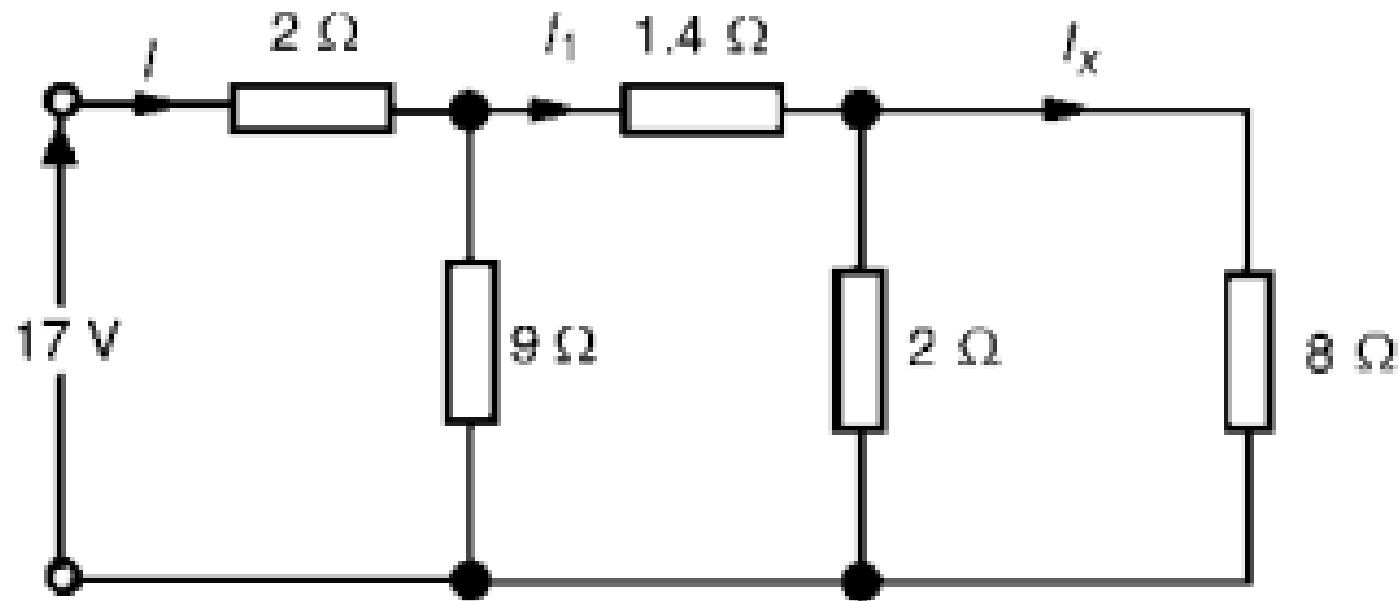
# EXAMPLE

- For the arrangement shown in Figure , find the current  $I_x$



# EXAMPLE

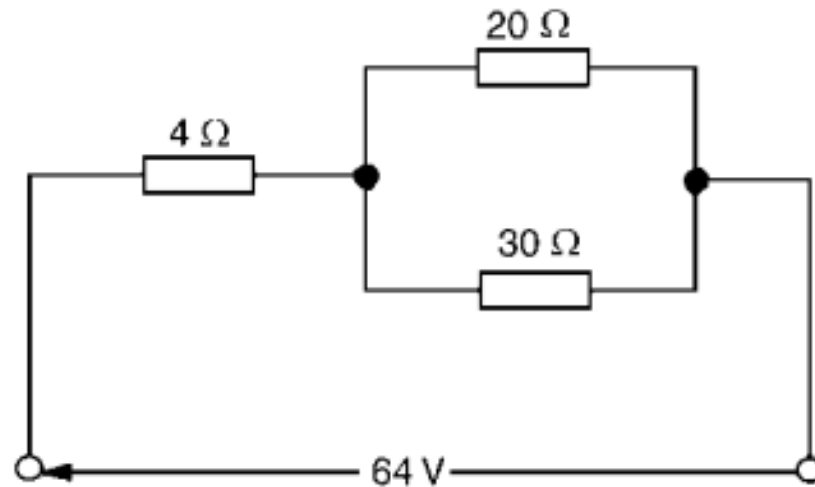
- (a) Calculate the current flowing in the  $30\ \Omega$  resistor shown in Figure
- (b) What additional value of resistance would have to be placed in parallel with the  $20\ \Omega$  and  $30\ \Omega$  resistors to change the supply current to  $8\text{ A}$ , the supply voltage remaining constant.



# Kirchhoff's (First) Current Law (KCL)

At any junction in an electric circuit the total current flowing towards that junction is equal to the total current flowing away from the junction,


i.e.  $\sum I = 0$

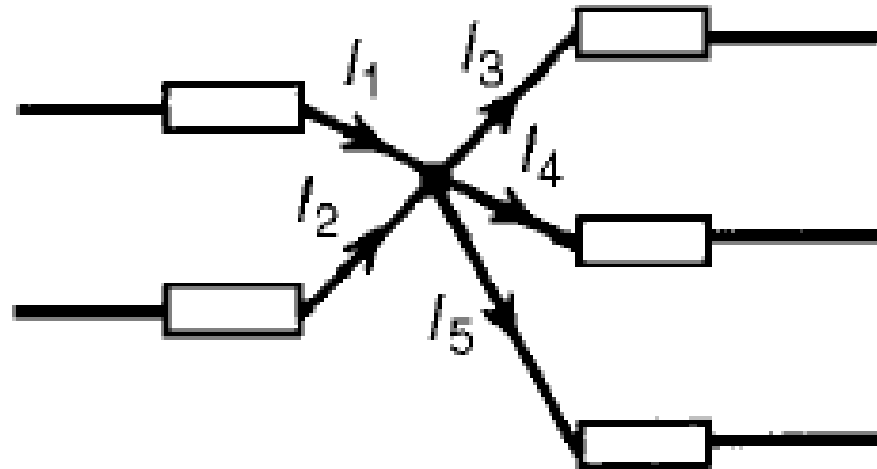

$$I_1 + I_2 = I_3 + I_4 + I_5 \quad \text{or} \quad I_1 + I_2 - I_3 - I_4 - I_5 = 0$$
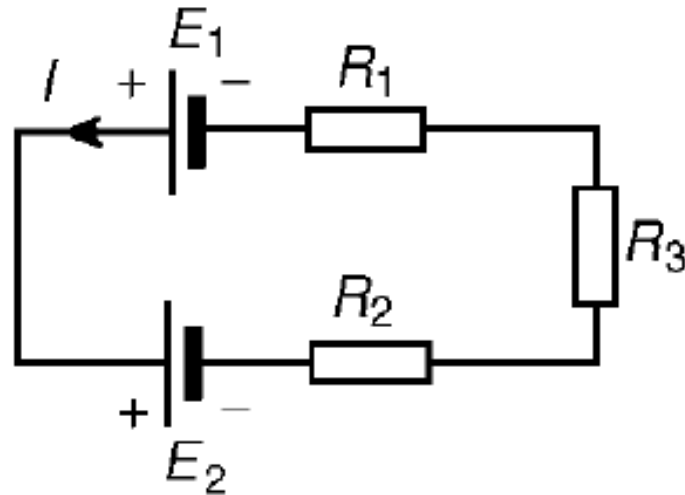
# Kirchhoff's (Second) Voltage Law


In any closed loop in a network, the algebraic sum of the voltage drops (i.e. products of current and resistance) taken around the loop is equal to the resultant e.m.f. acting in that loop.



$$E_1 - E_2 = IR_1 + IR_2 + IR_3$$
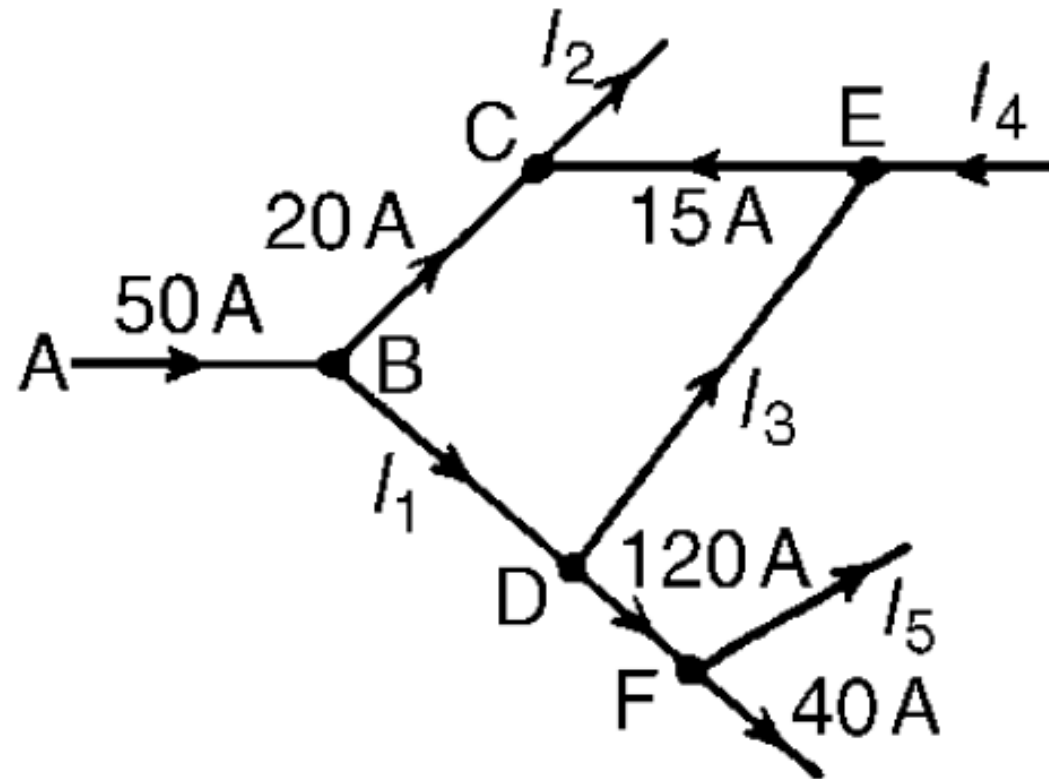
# KCL Example

Find the marked unknown currents in the figure.



# KCL Example

Applying Kirchhoff's current law:

For junction B:  $50 = 20 + I_1$ . Hence  $I_1 = 30$  A

For junction C:  $20 + 15 = I_2$ . Hence  $I_2 = 35$  A

For junction D:  $I_1 = I_3 + 120$

i.e.  $30 = I_3 + 120$ . Hence  $I_3 = -90$  A

(i.e. in the opposite direction to that shown in Figure :

For junction E:  $I_4 + I_3 = 15$


i.e.  $I_4 = 15 - (-90)$ . Hence  $I_4 = 105$  A

For junction F:  $120 = I_5 + 40$ . Hence  $I_5 = 80$  A


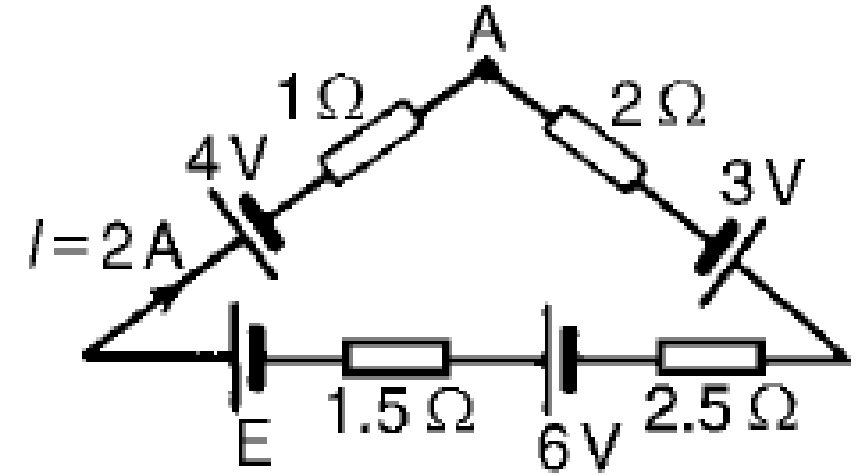
# KVL Example

Determine the value of e.m.f.  $E$  in the Figure.



Applying Kirchhoff's voltage law and moving clockwise around the loop of starting at point A:


$$\begin{aligned} 3 + 6 + E - 4 &= (I)(2) + (I)(2.5) + (I)(1.5) + (I)(1) \\ &= I(2 + 2.5 + 1.5 + 1) \end{aligned}$$

$$\text{i.e.} \quad 5 + E = 2(7), \text{ since } I = 2 \text{ A}$$

$$\text{Hence} \quad E = 14 - 5 = 9 \text{ V}$$

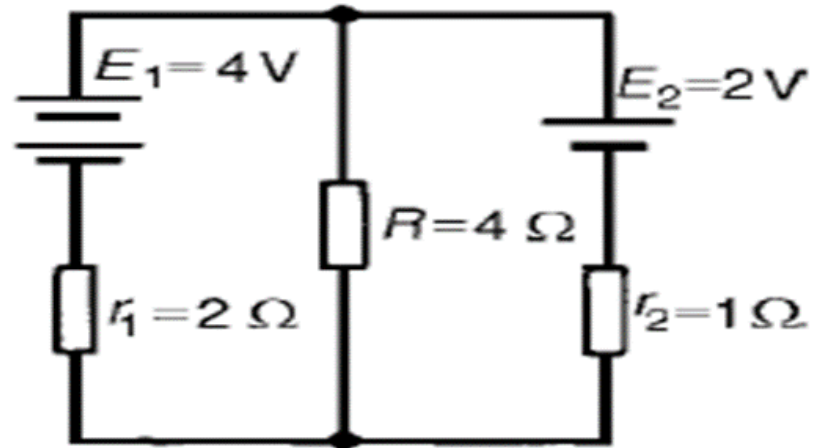
# KVL Example

- Determine the current flowing in each branch using Kirchhoff's current and voltage laws


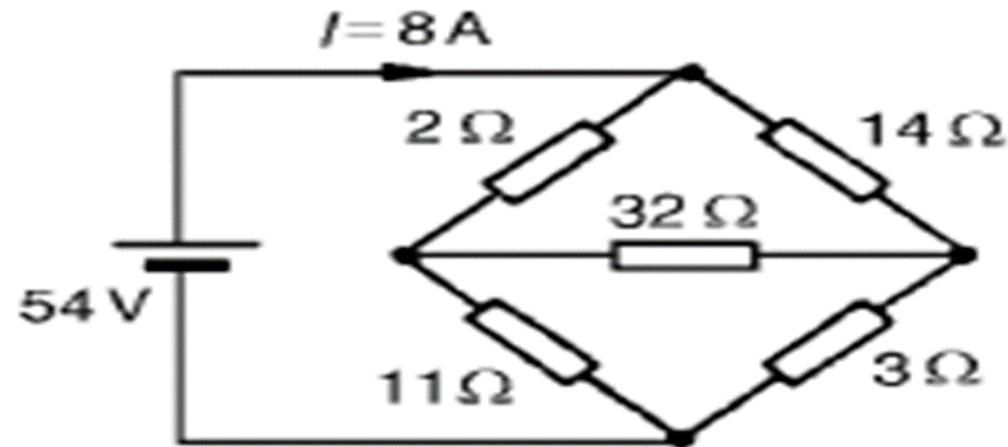
# KVL Example

- For the bridge network shown in the figure below, determine the current in each of the resistors



# Resistance Variation

The resistance of an electrical conductor depends on the following 4 factors,

- (a) the length of the conductor,
- (b) the cross-sectional area of the conductor,
- (c) the type of material and
- (d) the temperature of the material.

# Resistivity

- Resistance,  $R$ , is directly proportional to length,  $l$ , of a conductor, i.e.  $R \propto l$ .
- Resistance,  $R$ , is inversely proportional to cross-sectional area,  $a$ , of a conductor, i.e.  $R \propto 1/a$ .
- The constant of proportionality in this relationship is the type of material used and is known as the resistivity of the material and is given the symbol  $\rho$  (Greek rho). Thus,

- $\rho$  is measured in ohm-metres ( $\Omega\text{m}$ ) 
$$R = \frac{\rho l}{a} \text{ ohms}$$

# Typical values of resistivity

Material	$\rho$ ( $\Omega$ m) at 0 °C
Aluminium	$2.7 \times 10^{-8}$
Brass	$7.2 \times 10^{-8}$
Copper	$1.59 \times 10^{-8}$
Eureka	$49.00 \times 10^{-8}$
Manganin	$42.00 \times 10^{-8}$
Carbon	$6500.00 \times 10^{-8}$
Tungsten	$5.35 \times 10^{-8}$
Zinc	$5.37 \times 10^{-8}$

Problem 4. Calculate the resistance of a 2 km length of aluminium overhead power cable if the cross-sectional area of the cable is  $100 \text{ mm}^2$ . Take the resistivity of aluminium to be  $0.03 \times 10^{-6} \Omega\text{m}$

# Example

A coil is wound from a 10 m length of copper wire having a cross-sectional area of 1.0 mm<sup>2</sup>. Calculate the resistance of the coil. The resistivity of copper is 1.59 x 10<sup>-8</sup>

$$R = \rho \frac{l}{A} = \frac{1.59 \times 10^{-8} \times 10}{1 \times 10^{-6}} = 0.159 \, \Omega$$



# Temperature coefficient of resistance

- As the temperature of a material increases, most conductors increase in resistance, insulators decrease in resistance, whilst the resistance of some special alloys remain almost constant.
- The temperature coefficient of resistance of a material is the increase in the resistance of a  $1\ \Omega$  resistor of that material when it is subjected to a rise of temperature of  $1^\circ\text{C}$ .
- The symbol used for the temperature coefficient of resistance is  $\alpha$  (Greek alpha)
- The units are usually expressed as 'per  $^\circ\text{C}$ '.

# Temperature coefficient of resistance

- If the resistance of a material at  $0^{\circ}\text{C}$  is known the resistance at any other temperature can be determined from:

$$R_{\theta} = R_0(1 + \alpha_0\theta)$$

where

$R_0$  = resistance at  $0^{\circ}\text{C}$

$R_{\theta}$  = resistance at temperature  $\theta^{\circ}\text{C}$

$\alpha$  = temperature coefficient of resistance at  $0^{\circ}\text{C}$

- If a material having a resistance  $R_0$  at  $0^{\circ}\text{C}$ , taken as the standard temperature, has a resistance  $R_1$  at  $\theta_1$  and  $R_2$  at  $\theta_2$ , and if  $\alpha_0$  is the temperature coefficient of resistance at  $0^{\circ}\text{C}$ , then

$$\frac{R_1}{R_2} = \frac{(1 + \alpha_0\theta_1)}{(1 + \alpha_0\theta_2)}$$

# Temperature coefficient of resistance

- If the resistance of a material at room temperature (approximately 20°C),  $R_{20}$ , and the temperature coefficient of resistance at 20°C,  $\alpha_{20}$ , are known then the resistance  $R_\theta$  at temperature  $\theta$  °C is given by:

$$R_\theta = R_{20}[1 + \alpha_{20}(\theta - 20)]$$

# Typical temperature coefficients of resistance referred to 0 °C

- Some materials such as carbon have a negative temperature coefficient of resistance,
- i.e. their resistances fall with increase in temperature.

Material	$\alpha_0$ (/°C) at 0 °C
Aluminium	0.003 81
Copper	0.004 28
Silver	0.004 08
Nickel	0.006 18
Tin	0.004 4
Zinc	0.003 85
Carbon	−0.000 48
Manganin	0.000 02
Constantan	0
Eureka	0.000 01
Brass	0.001

# Example

A coil of copper wire has a resistance of  $100\ \Omega$  when its temperature is  $0^\circ\text{C}$ . Determine its resistance at  $70^\circ\text{C}$  if the temperature coefficient of resistance of copper at  $0^\circ\text{C}$  is  $0.0043/^\circ\text{C}$

$$\text{Resistance } R_\theta = R_0(1 + \alpha_0\theta)$$

$$\begin{aligned}\text{Hence resistance at } 70^\circ\text{C}, R_{70} &= 100[1 + (0.0043)(70)] \\ &= 100[1 + 0.301] = 100(1.301) \\ &= \mathbf{130.1\ \Omega}\end{aligned}$$

# Example

A coil of copper wire has a resistance of 10  $\Omega$  at 20°C. If the temperature coefficient of resistance of copper at 20°C is 0.004/°C determine the resistance of the coil when the temperature rises to 100°C

$$\text{Resistance at } \theta^{\circ}\text{C, } R = R_{20}[1 + \alpha_{20}(\theta - 20)]$$

$$\begin{aligned}\text{Hence resistance at } 100^{\circ}\text{C, } R_{100} &= 10[1 + (0.004)(100 - 20)] \\ &= 13.2 \Omega\end{aligned}$$

# Homework

When a potential difference of 10 V is applied to a coil of copper wire of mean temperature 20 °C, a current of 1.0 A flows in the coil. After some time the current falls to 0.95 A yet the supply voltage remains unaltered. Determine the mean temperature of the coil given that the temperature coefficient of resistance of copper is  $4.28 \times 10^{-3}/^{\circ}\text{C}$  referred to 0 °C.